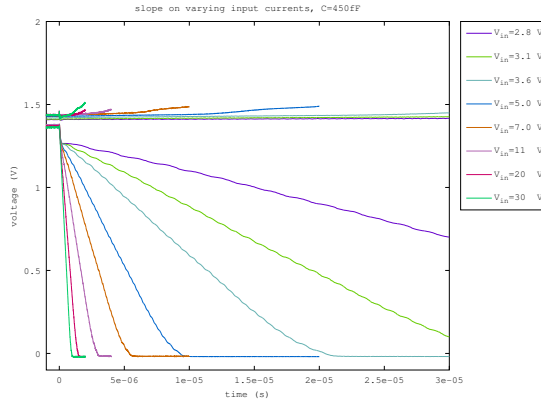


Preethi's ROIC analysis


Kees Kroep 4246373

August 25, 2016


1 normal mode




(a) $C = 450$ fF

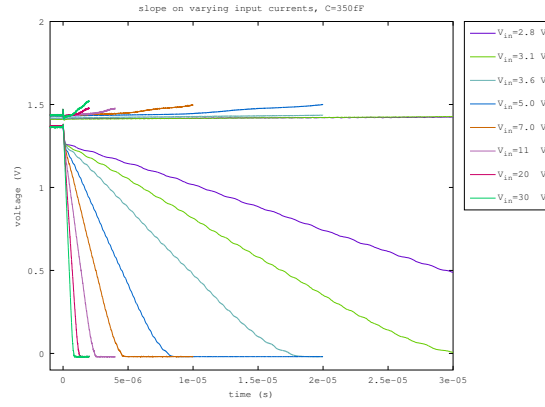

(b) $C = 350$ fF

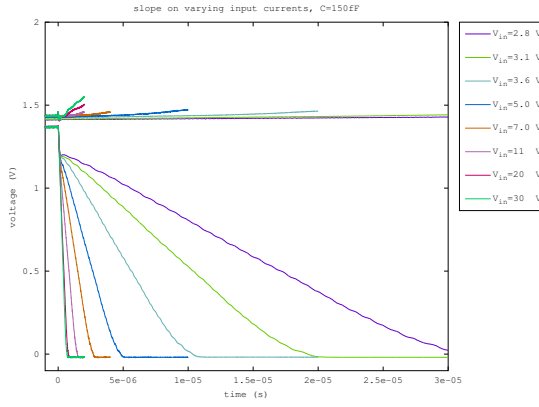


(c) $C = 150$ fF

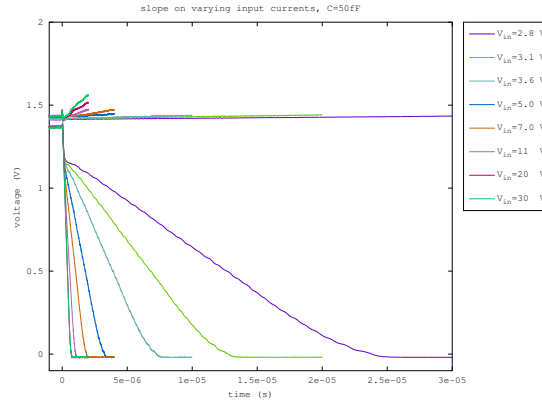


(d) $C = 50$ fF


Figure 1: Expected versus measured charge up times for different input voltages. The input voltage is connected to the input through a resistor of 20 M Ω

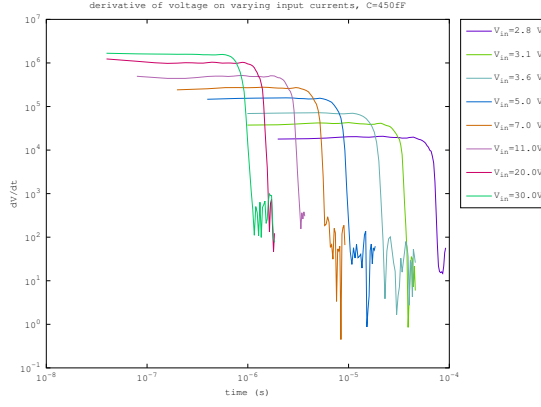


(a) $C = 450 \text{ fF}$

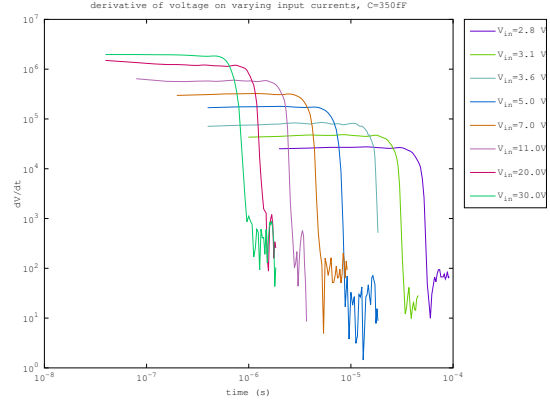

(b) $C = 350 \text{ fF}$

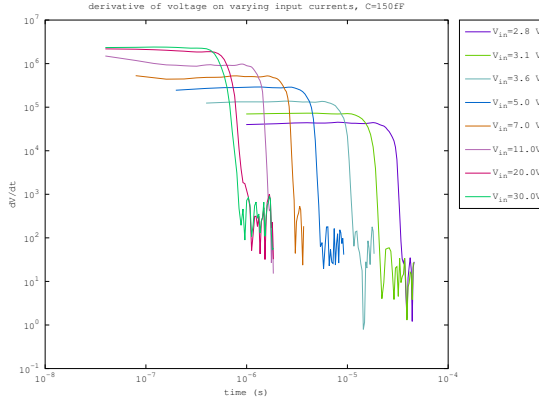


(c) $C = 150 \text{ fF}$

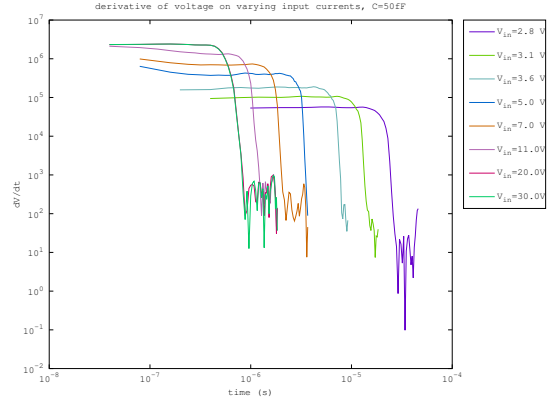


(d) $C = 50 \text{ fF}$


Figure 2: The plot shows dv/dt against time. The plot is in log scale, which allows for an easy read on the maximum slope and the time needed to discharge the integrator capacitance.

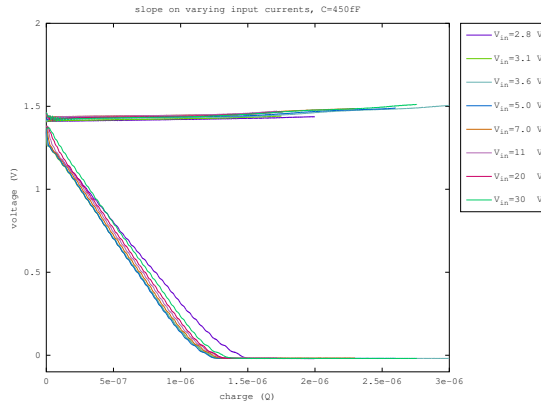


(a) $C = 450 \text{ fF}$

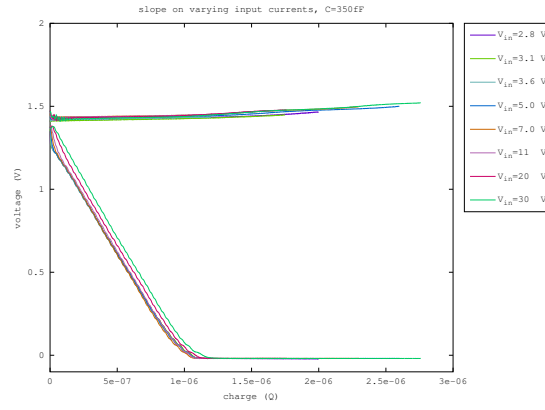

(b) $C = 350 \text{ fF}$

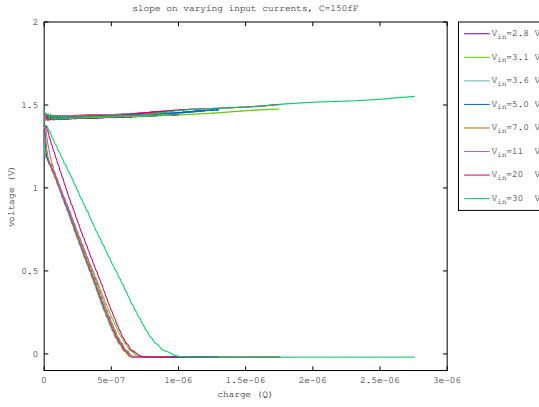


(c) $C = 150 \text{ fF}$

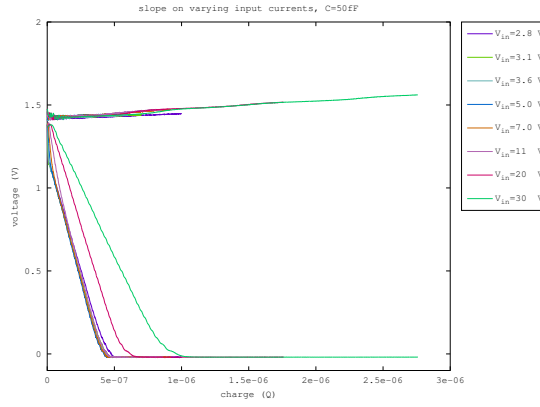


(d) $C = 50 \text{ fF}$


Figure 3: This plot is showing charge versus voltage

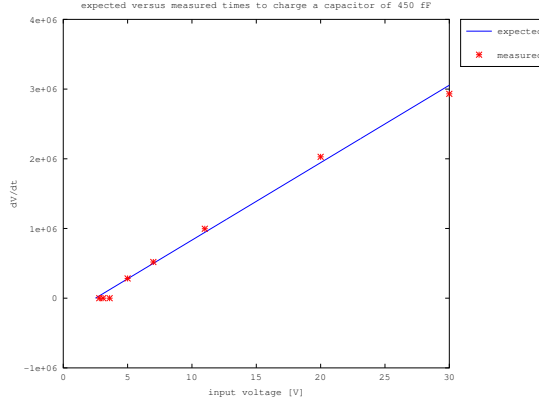


(a) $C = 450 \text{ fF}$

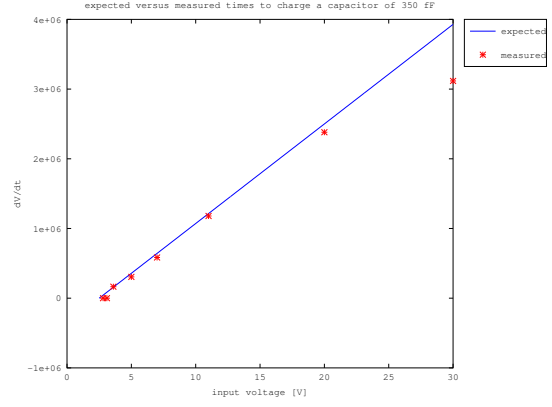

(b) $C = 350 \text{ fF}$

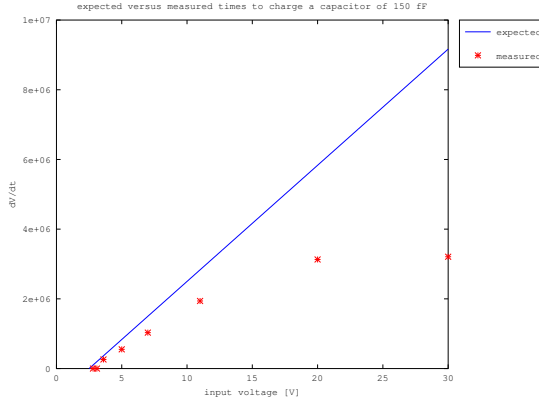

(c) $C = 150 \text{ fF}$

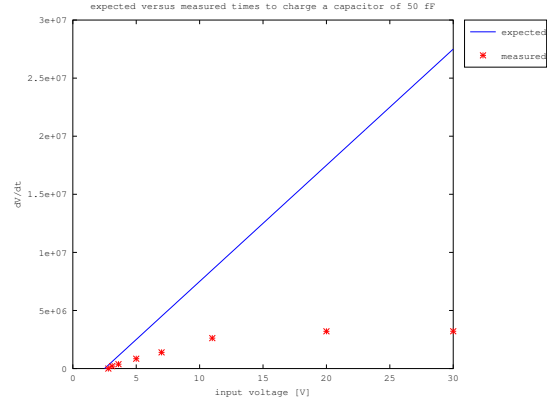


(d) $C = 50 \text{ fF}$


Figure 4: Expected versus measured charge up times for different input voltages. The input voltage is connected to the input through a resistor of $20 \text{ M}\Omega$.

2 large current focussed

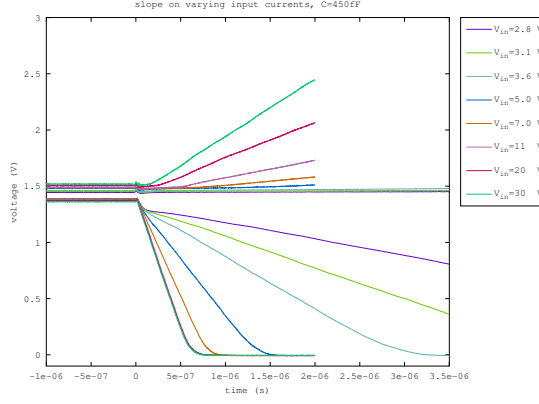
In this section the $20\text{ M}\Omega$ input resistor is replaced with a $4\text{ M}\Omega$ resistor.




(a) $C = 450\text{ fF}$

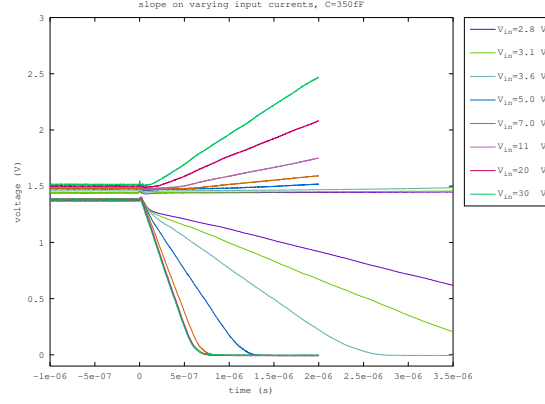

(b) $C = 350\text{ fF}$

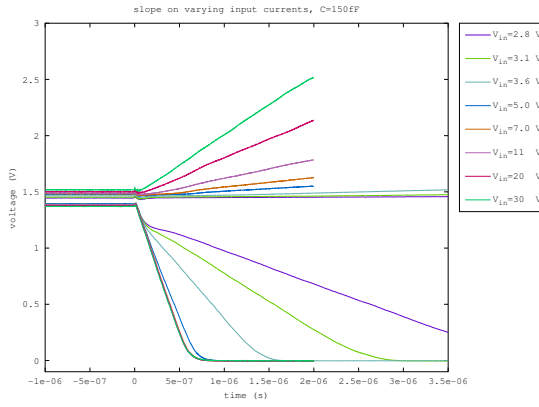


(c) $C = 150\text{ fF}$

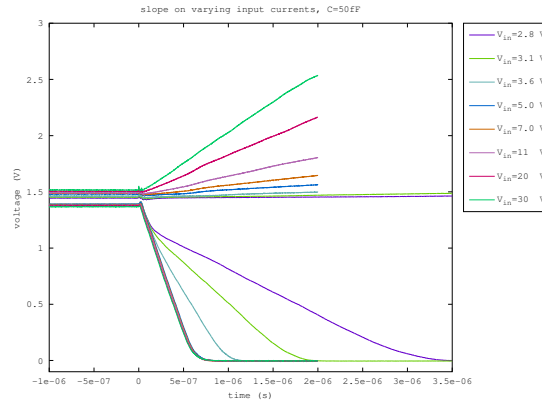


(d) $C = 50\text{ fF}$


Figure 5: Expected versus measured charge up times for different input voltages. The input voltage is connected to the input through a resistor of $4\text{ M}\Omega$

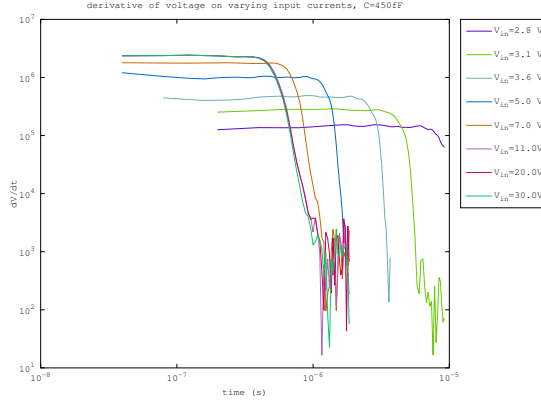


(a) $C = 450 \text{ fF}$

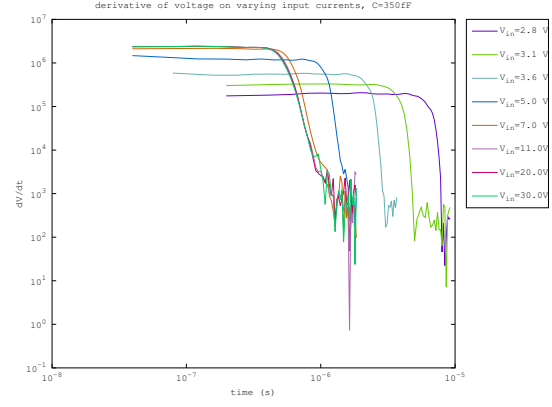

(b) $C = 350 \text{ fF}$

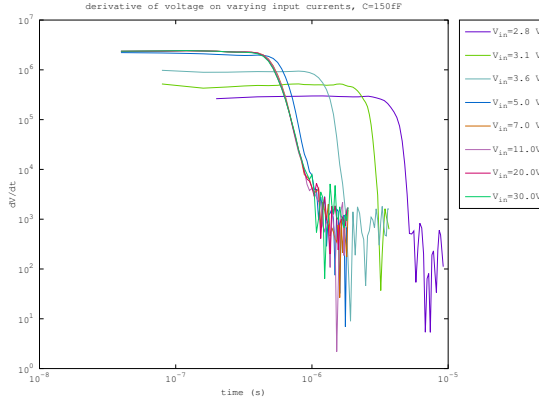


(c) $C = 150 \text{ fF}$

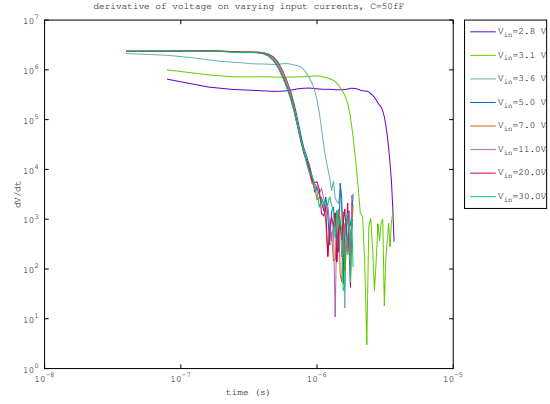


(d) $C = 50 \text{ fF}$


Figure 6: The plot shows dv/dt against time. The plot is in log scale, which allows for an easy read on the maximum slope and the time needed to discharge the integrator capacitance.

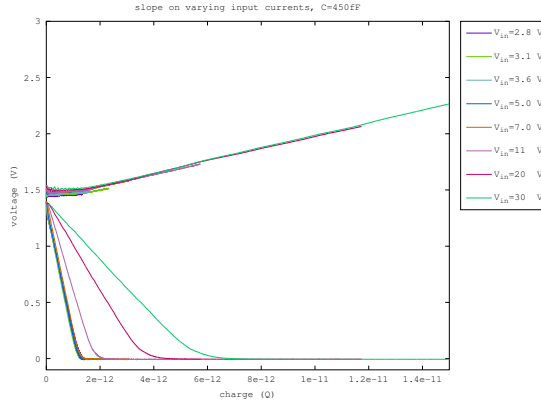


(a) $C = 450 \text{ fF}$

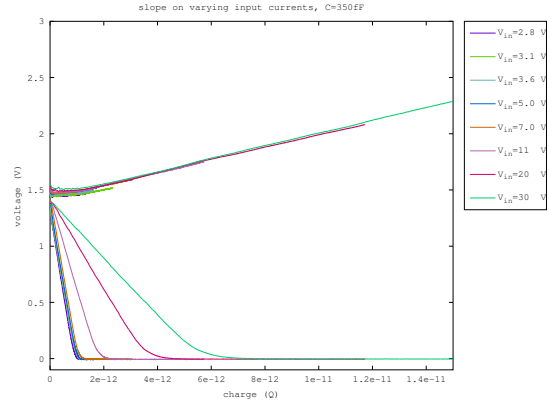

(b) $C = 350 \text{ fF}$

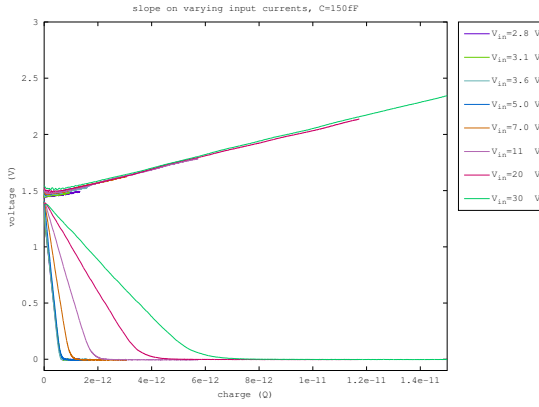


(c) $C = 150 \text{ fF}$

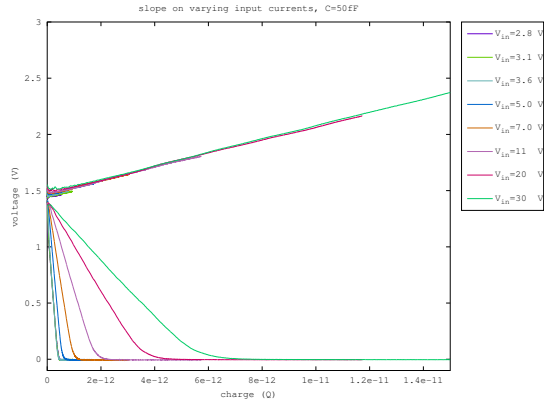


(d) $C = 50 \text{ fF}$


Figure 7: This plot is showing charge versus voltage

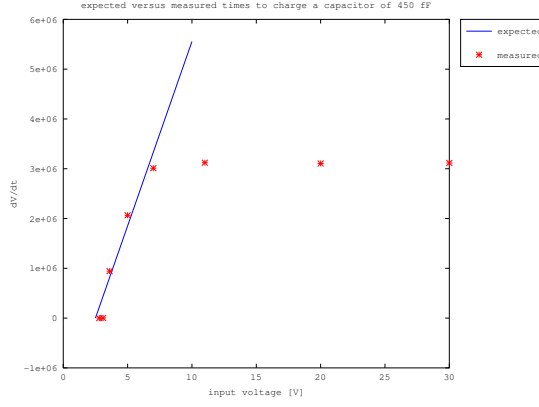


(a) $C = 450 \text{ fF}$

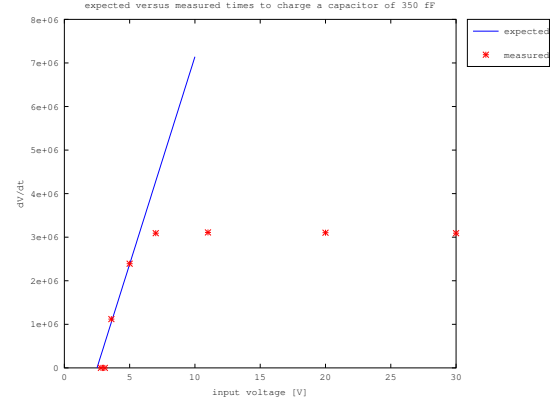

(b) $C = 350 \text{ fF}$

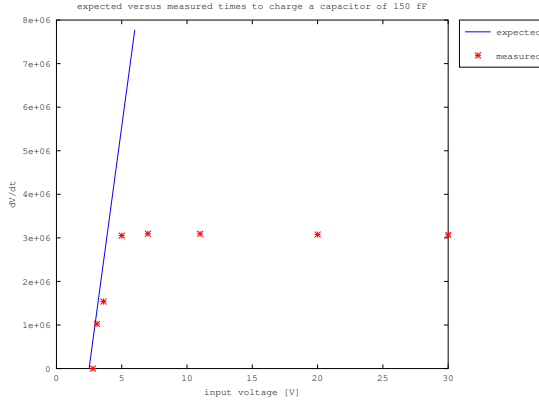


(c) $C = 150 \text{ fF}$

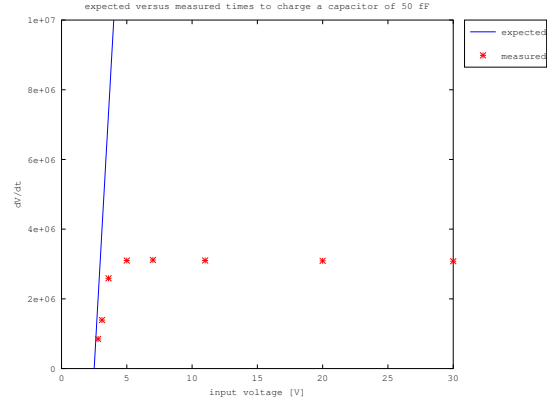


(d) $C = 50 \text{ fF}$

Figure 8: Expected versus measured charge up times for different input voltages. The input voltage is connected to the input through a resistor of $4 \text{ M}\Omega$.


3 vbo focussed

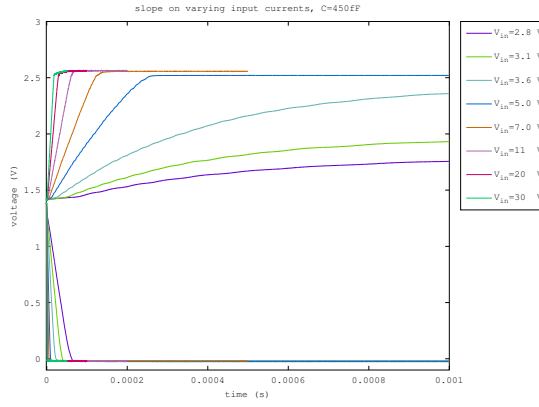


(a) $C = 450 \text{ fF}$

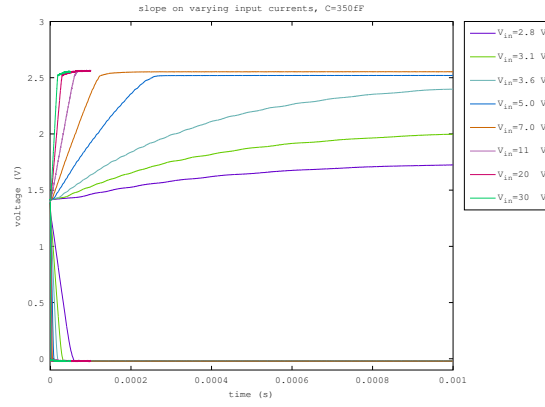

(b) $C = 350 \text{ fF}$

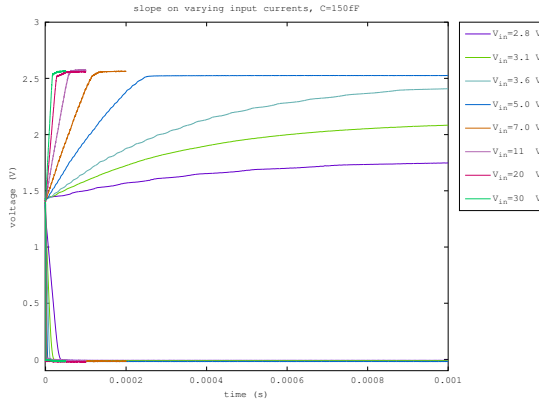


(c) $C = 150 \text{ fF}$

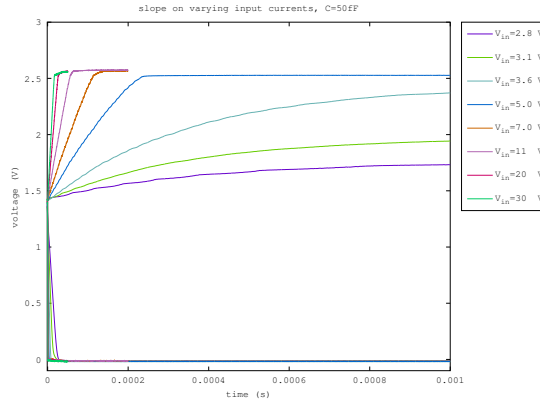


(d) $C = 50 \text{ fF}$


Figure 9: Expected versus measured charge up times for different input voltages. The input voltage is connected to the input through a resistor of $20 \text{ M}\Omega$

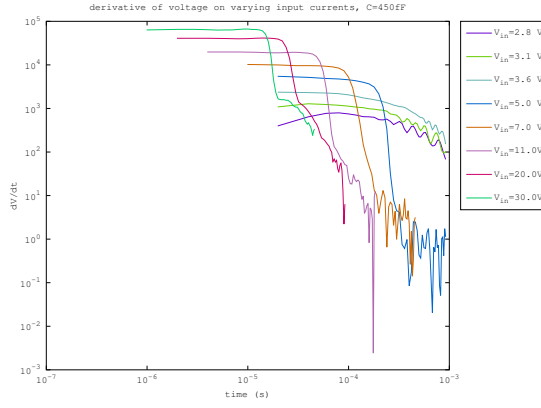


(a) $C = 450 \text{ fF}$

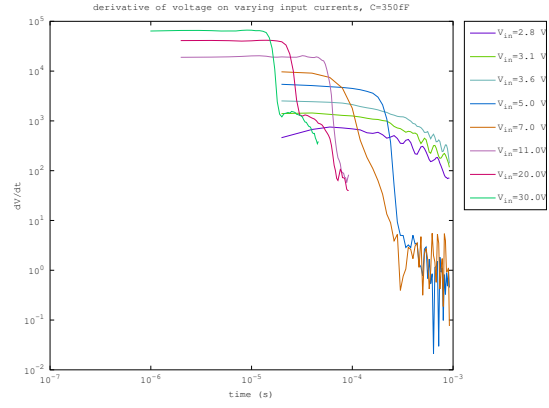

(b) $C = 350 \text{ fF}$

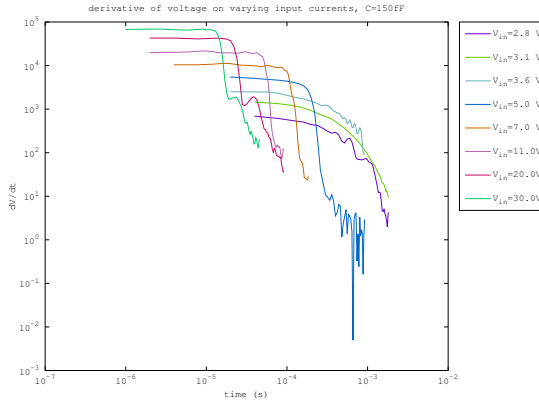


(c) $C = 150 \text{ fF}$

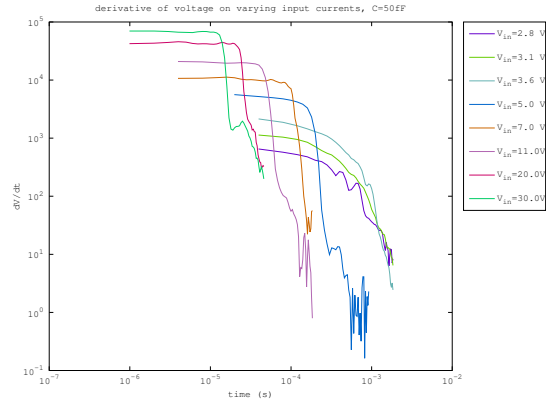


(d) $C = 50 \text{ fF}$


Figure 10: The plot shows dv/dt against time of the vbo.

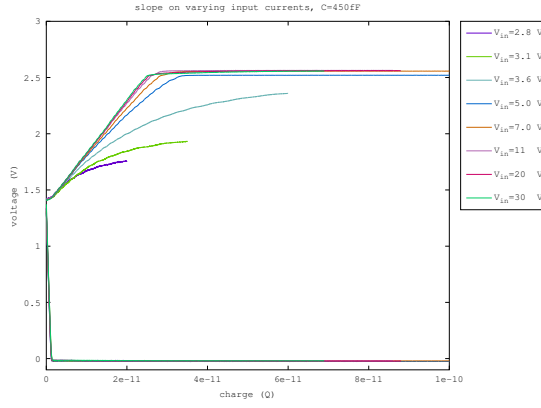


(a) $C = 450 \text{ fF}$

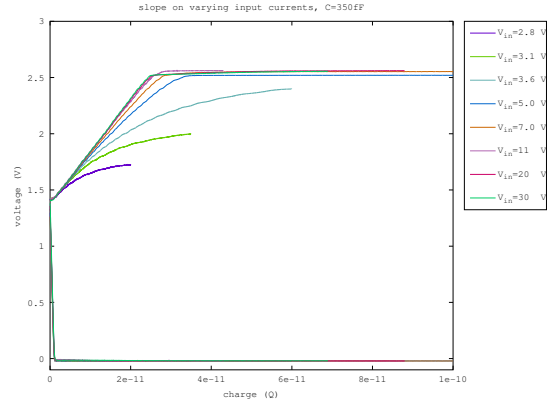

(b) $C = 350 \text{ fF}$

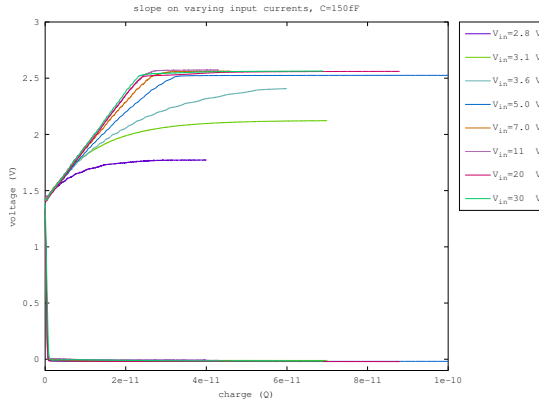


(c) $C = 150 \text{ fF}$

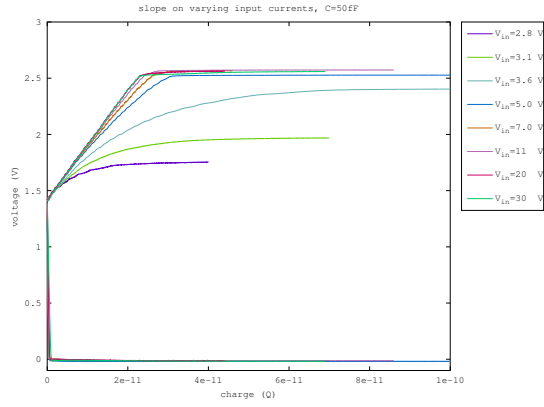


(d) $C = 50 \text{ fF}$


Figure 11: This plot is showing charge versus voltage

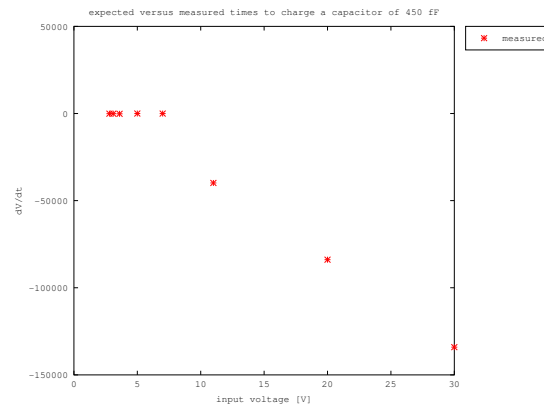


(a) $C = 450 \text{ fF}$

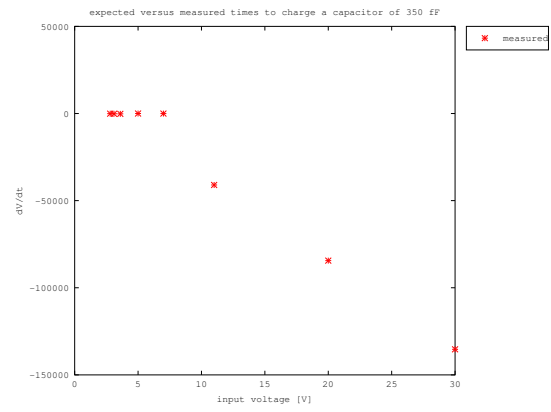

(b) $C = 350 \text{ fF}$

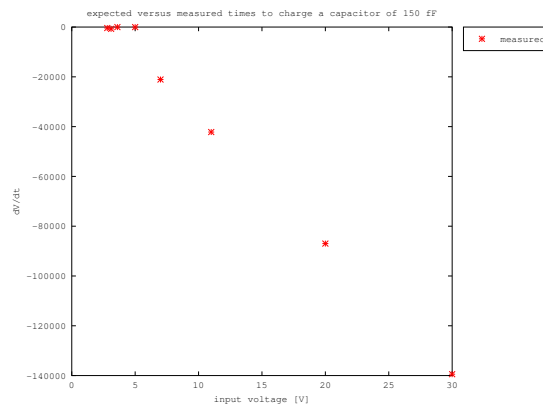

(c) $C = 150 \text{ fF}$

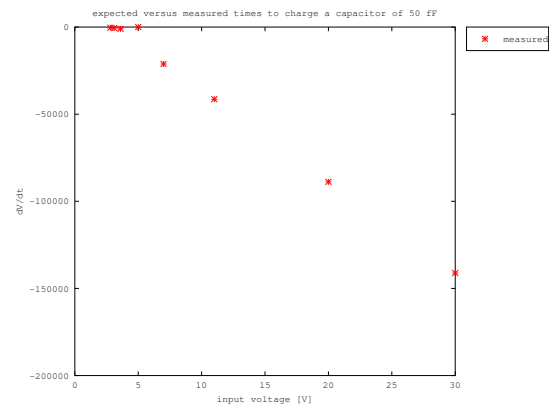

(d) $C = 50 \text{ fF}$

Figure 12: charge times of vbo for different input voltages. The input voltage is connected to the input through a resistor of $20 \text{ M}\Omega$.